

Simulation:

Minimum cycle time: 6.0ns


Design strategy: pipeline

Circuit diagram:


Gate level circuit diagram:

Building blocks:

 
**MUXP(BW)**: basically BW MUX21s sharing the same CTRL.





**FAP(BW)**: BW-bit full-adder

 


, which is denoted as:

 

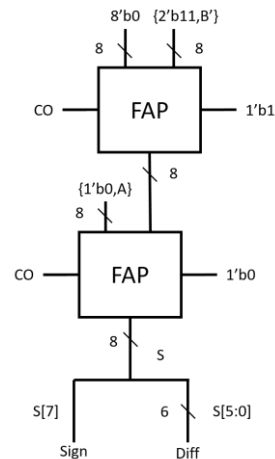 
**SUB76**: subtract a 6-bit unsigned number B from a 7-bit unsigned number, then produce a sign bit and a 6-bit unsigned difference.




notation:

 

 
**SUB65:** subtract a 5-bit unsigned number B from a 6-bit unsigned number, then produce a sign bit and a 6-bit unsigned difference.




notation:

 

 
**Shifter:** multiply a 5-bit number by 2, then produce a 6-bit product.



Notation:

 

First stage ( $k=1$ ) :

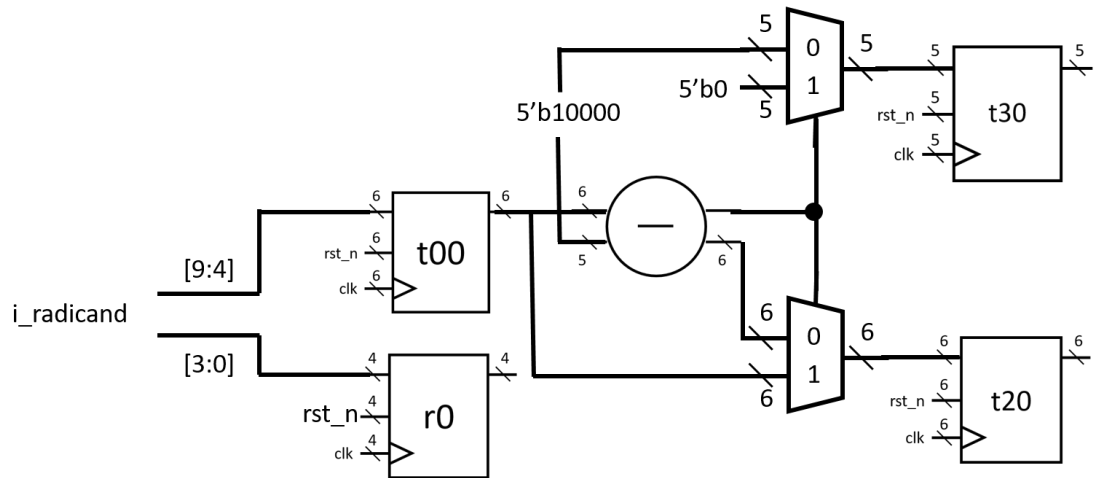

Discussion:

在這次的作業中, 我使用了 pipeline strategy, 而數學上則是使用了長除法開根號的思維:  $(a+b)^2 = a^2 + b(b+2a)$ ; 在數位電路實作上必須將我們熟悉的十進位改成二進位制, 所以這個演算法的核心就是:  $t_3(\text{square root})$  增加  $2^{(5-k)}$ , radicant 就會增加  $2^{(5-k)} * (2^{(5-k)} + 2 * t_3)$ ; 我們就是如此一位一位地往下比, 若剩餘的 radicant 還足夠減去  $2^{(5-k)} * (2^{(5-k)} + 2 * t_3)$ , 則 square root 就增加  $2^{(5-k)}$ , 這樣一來, 做完第五個 stage 的  $t_3$  就是我們要的 square root 啦。

而為了減少 transistor 數量, 這次我參考了相關的論文, 發現在數學上可以證明每個 stage 只會用到 radicant 的 6bit, 而且之前用過的就不會再用到, 不用浪費記憶體保存, 因此在  $t_2$  與  $r$  的設計上就省去非常多不必要的 flip flop.

另外, 原本有考慮像第三次作業一樣做比較器, 但後來發現減法器是決定 critical path 最重要的因素, 就算比完不用減也還要等其他 stage 減法器, 因此改成直接用減法器產生 sign bit, 藉此判斷大小, 也縮短了 critical path.

#### Reference:

A New Algorithm for Designing Square Root Calculators based on FPGA with Pipeline Technology (Xiumin Wang, Yang Zhang, Qiang Ye, Shihua Yang)